


Static Timing Analysis (STA)

Static Timing Analysis (STA)

- **STA** is a technique for digital design verification. It:
 - ❑ Validates if the design can operate at the set timing constraints
 - ❑ Is a complete and exhaustive verification of all timing checks of a design
 - ❑ Is used instead of simulation

Simulation

 
- Simulating (dynamically) circuit response for a specified set of input patterns
 - Circuit modeled as network of capacitors, resistors and voltage/current sources



STA (2)

- Vector-less topological analysis of a circuit.

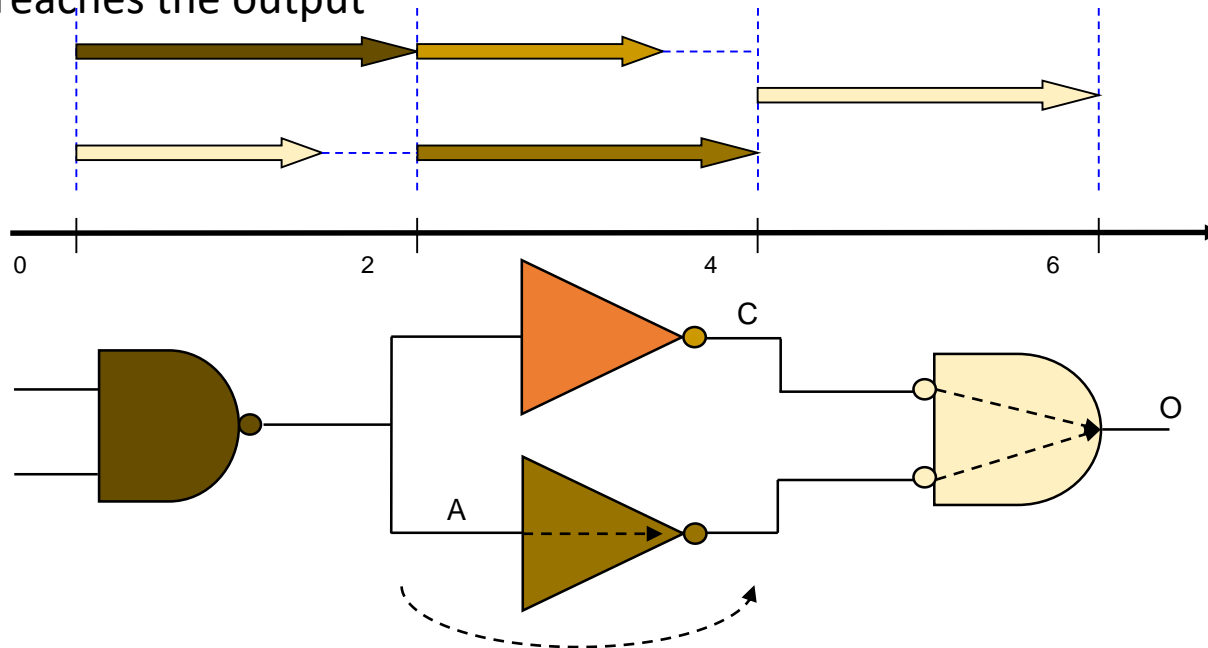- The signal at the input is propagated through the gates at each level till it reaches the output



STA vs. Simulation

Simulation

■ Advantages

- Can be very accurate (Spice-level)

■ Disadvantages

- Analysis quality depends on stimulus vectors
- Non-exhaustive, slow

Static Timing Analysis (STA)

■ Advantages

- Exhaustive timing coverage
- Does not require input vectors
- Faster operation

■ Disadvantages

- Less accurate
- Must define timing requirements/exceptions
- Difficulty in handling asynchronous designs, false paths

Digital Circuits Timing Goals

- Achievement of required frequency
 - Digital circuits are constrained to work under specific frequencies
 - All separate parts of circuit are constrained to have delay smaller than clock period
- Meeting timing constraints
 - Avoiding collision of signals
 - Avoiding failure
- STA verifies these


Components of Circuit Timing

- Delay components

- Cells, Interconnects





- Constrained components

 - Clocked registers require setup/hold, recovery/removal constraints





For circuit to operate without failure it is **required** that delay components at no point violate constraints of other components.

Cell Timing Parameters

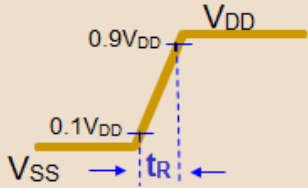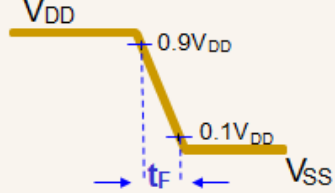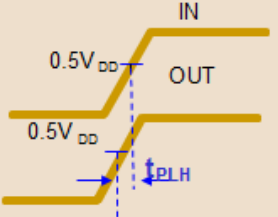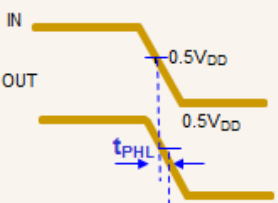N	Parameter	Unit	Symbol	Figure	Definition
1.	Rise transition time	ns	t_R		The time it takes a driving pin to make a transition from kV_{DD} to $(1-k)V_{DD}$ value. Usually $k=0.1$ (also possible $k=0.2, 0.3$, etc)
2.	Fall transition time	ns	t_F		The time it takes a driving pin to make a transition from $(1-k)V_{DD}$ to kV_{DD} value. Usually $k=0.1$ (also possible $k=0.2, 0.3$, etc)
3.	Propagation delay low-to-high (rise)	ns	t_{PLH} (t_{PR})		Time difference between the input signal crossing a $0.5V_{DD}$ and the output signal crossing its $0.5V_{DD}$ when the output signal is changing from low to high
4.	Propagation delay high-to-low (Fall)	ns	t_{PHL} (t_{PF})		Time difference between the input signal crossing a $0.5V_{DD}$ and the output signal crossing its $0.5V_{DD}$ when the output signal is changing from high to low

Cell Timing Constraints


Setup/Hold, Recovery/Removal Constraints

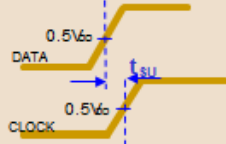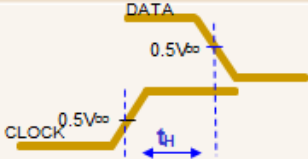N	Parameter	Unit	Symbol	Figure	Definition
1	Setup time (only for flip-flops or latches)	ns	t_{SU}		The minimum period in which the input data to a flip-flop or a latch must be stable before the active edge of the clock occurs
2	Hold time (only for flip-flops or latches)	ns	t_H		The minimum period in which the input data to a flip-flop or a latch must remain stable after the active edge of the clock has occurred

Timing Closure Problem

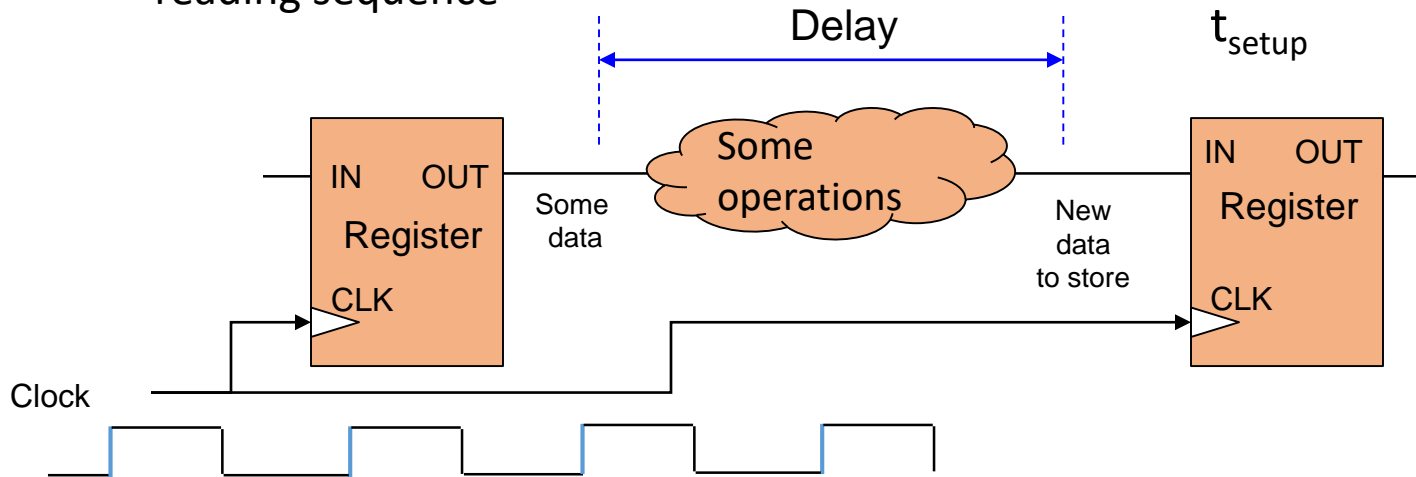- Problem

- In clocked environment signals on the register inputs must arrive before next reading sequence



Clock: Both registers store new value at specific points of time (with some frequency, like 1GHz)

$$\text{Delay} + t_{\text{setup}} < T_{\text{clock}}$$

Static Timing Analysis Steps


Circuit is broken into timing paths



Delay of each path is calculated



 For each path delays are checked against timing constraints



Path	Delay	Constraint
a → c	?	?
b → c	?	?
clock → d	?	?
clock → y	?	?

STA Concepts


- Timing Path
- Required Time
- Arrival Time
- Slack
- Critical Path

Timing Paths

- Timing path has a start point and an endpoint.


- Start point:

- Input ports
- Clock pins of flip-flops

 


- Endpoints:

 - Output ports
- data input pins of flip-flops




Possible Paths

 

Paths
$a \rightarrow \text{MUX1.0} \rightarrow \text{MUX2.0} \rightarrow \text{out}$
$a \rightarrow \text{MUX1.0} \rightarrow \text{MUX2.1} \rightarrow \text{out}$
$b \rightarrow \text{MUX1.1} \rightarrow \text{MUX2.0} \rightarrow \text{out}$
$b \rightarrow \text{MUX1.1} \rightarrow \text{MUX2.1} \rightarrow \text{out}$

False Paths

 
- Paths which physically exist in a design but are not logic paths. These paths never get sensitized under any input condition



Paths
$a \rightarrow \text{MUX1.0} \rightarrow \text{MUX2.0} \rightarrow \text{out}$
$a \rightarrow \text{MUX1.0} \rightarrow \text{MUX2.1} \rightarrow \text{out}$
$b \rightarrow \text{MUX1.1} \rightarrow \text{MUX2.0} \rightarrow \text{out}$
$b \rightarrow \text{MUX1.1} \rightarrow \text{MUX2.1} \rightarrow \text{out}$


Multi-cycle Paths

 - There are data paths that require more than one clock period for execution.




Required Time

- **Required time** specifies the time point (interval) at which data is required to arrive at end point (data is required to be stable after arrival).
 - Time point after which data can become unstable (change) is called earliest required time
 - Time point after which data cannot become unstable (change) is called latest required time
- The requirement is set by timing constraints like setup/hold, removal/recovery, etc.

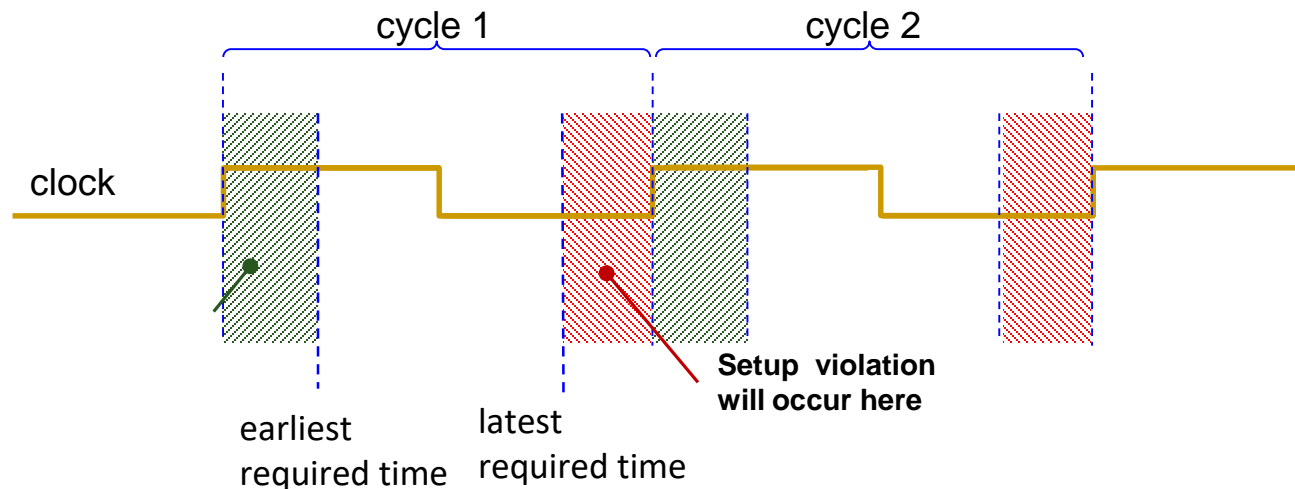



Arrival Time

 - Arrival time defines the time interval during which a data signal will arrive at a path endpoint (after arrival time signal will be stable).
- Data is normally triggered by clock edge
- Data arrival depend on circuit delay, which vary (depend on temperature, supply voltage, etc.)
- Minimum delay, early arrival
- Maximum delay, late arrival





Slack and Critical Path

  - **Slack** is the difference between the required time and the arrival time.
 - ❑ Negative slack → violation
 - ❑ Positive slack → constraints have been met
 - ❑ Critical path is a path in the design that has smallest slack





Early and Latest Analysis

  - STA tool calculates the slack of each logic path, in order to find critical path.
- Early and Latest analysis approaches:
 - Assumes circuits have minimum delay, compares arrival time to earliest required time (hold check)
 - Assumes circuits have maximum delay, compares arrival time to latest required time (setup check)



Path Groups

  - Timing paths are grouped into path groups by the clocks controlling their endpoints
- Slack is calculated in relation to each clock



Thank You